

Intro to Sensors Outline, Class 2

Daniel Bergey & Christalee Bieber

- Introduction (15 minutes)
 - orientation to handout
 - brief review of Class 1
- BJT Power Amp (30 minutes)
 - rules transistors follow in circuits
 1. $V_E = V_B - 0.6V$
 2. $I_{CE} = h * I_{BE}$ ($h \sim 100$)
 - Review: voltage follower circuit
 - Activity: current source circuit
- Input Conditioning (10 minutes)
 - read the documentation for I-V curves
 - Concept: think about the range of inputs you're going to get (e.g. temperature), and outputs you want (what are you driving?)
- Op-Amps (55 minutes)
 - how to insert DIP components into breadboards
 - Concept: open-loop vs. closed-loop configuration
Op-amp multiplies the difference between its inputs. But we never use them open-loop.
 - Activity: tuning gain with resistors
 - Activity: comparator to subtract constant voltage
 - Concept: why build these complex circuits?
- Wrap-up (10 minutes)